

ELECENG 3EJ4 Lab 3

Raeed Hassan
hassam41
McMaster University


December 12, 2020

Part 1

- Q1. 1. The relationship between I_o and I_{REF} is dependent on the EBJ area of the two BJTs. As the two BJTs are the same, they have the same EBJ area and the relationship between I_o and I_{REF} can be described as:

$$I_o = I_{REF}$$

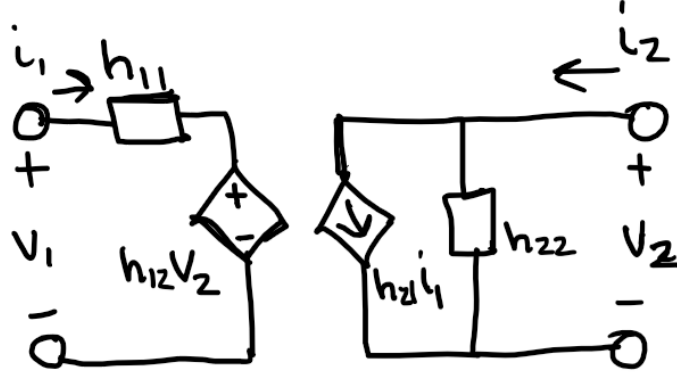2. When I_{REF} is 1 mA, I_o is equal to 0.975 mA, or $0.975I_{REF}$.
3. The values of I_o at $I_{REF} = 0.1$ mA and 1 mA are $1.04I_{REF}$ and $0.975I_{REF}$. The theoretical prediction and simulated results are similar, as the simulated results show that $I_o \approx I_{REF}$.
- Q2. 1. The input impedance R_{in} is 389.12 Ω . The current gain A_i is 1.042.
2. The output resistance R_o is 1.58 M Ω .
3. The linear two-port network for the current mirror is shown in Figure 1.



$$h_{11} = R_{in} = 389.12 \Omega$$

$$h_{22} = 1/R_o = 6.33 \times 10^{-7} \text{ S}$$

$$h_{21} = A_i = 1.042$$

$$h_{12} = \frac{v_{in}}{10^{-6}} \Rightarrow 7.05 \times 10^{-7} \text{ (100 Hz)} - 1.41 \times 10^{-6} \text{ (200 Hz)}$$

Figure 1: Linear two-port network for the current mirror using its h -parameters

Part 2

- Q3.** 1. The voltage gain A_d is 70.07 dB.
2. The measured voltage gain A_d is 58.1 dB. There was a slight mismatch. The offset voltage applied at V_2 was 1 mV.
- Q4.** The upper 3-dB frequency f_H is approximately 11.2 kHz.
- Q5.** The upper 3-dB frequency f_{3dB} of the differential amplifier using resistive loads in Lab 2 was 8.4 MHz, much greater than the differential amplifier with a current mirror in this lab. The differential amplifier with the current mirror load has a smaller f_{3dB} due to the internal capacitive effects of the BJTs used in the current mirror load.
- Q6.** The gain-bandwidth product of the differential amplifier with the current mirror load is 151.1, while the gain-bandwidth product of the differential amplifier with the resistive load is 152.0.

Appendix

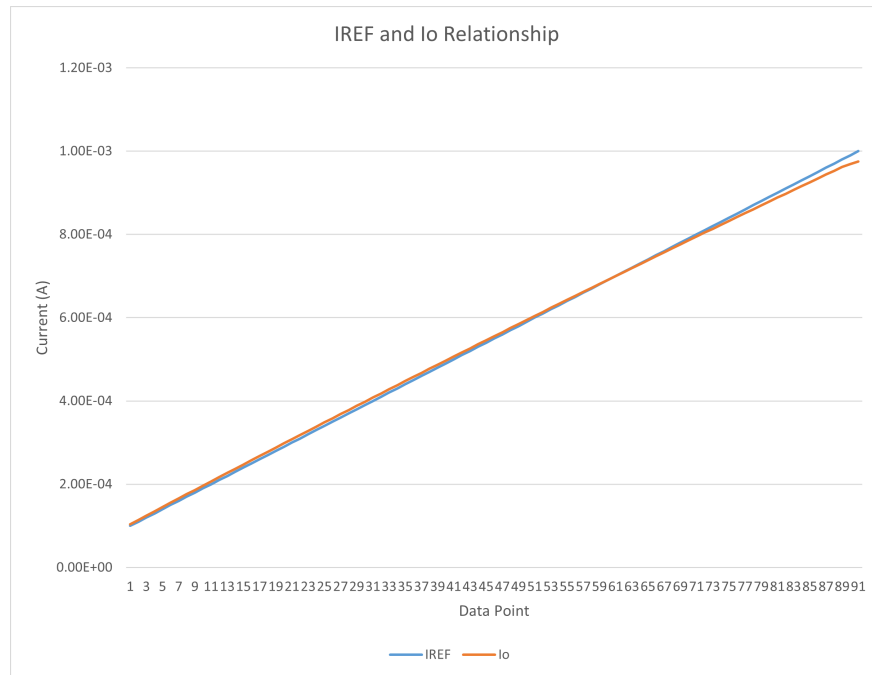


Figure 2: Step 1.2

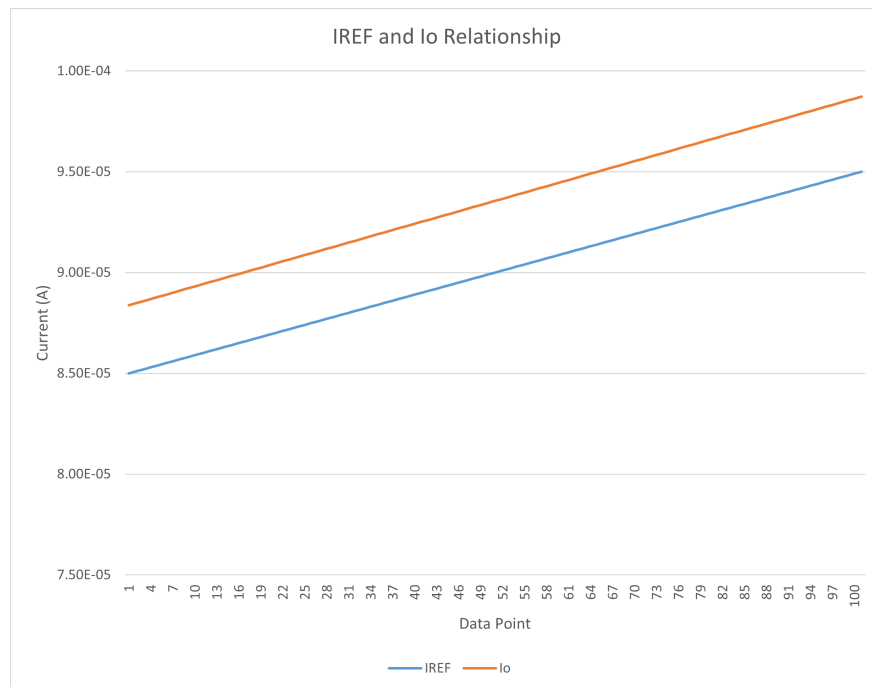


Figure 3: Step 1.3

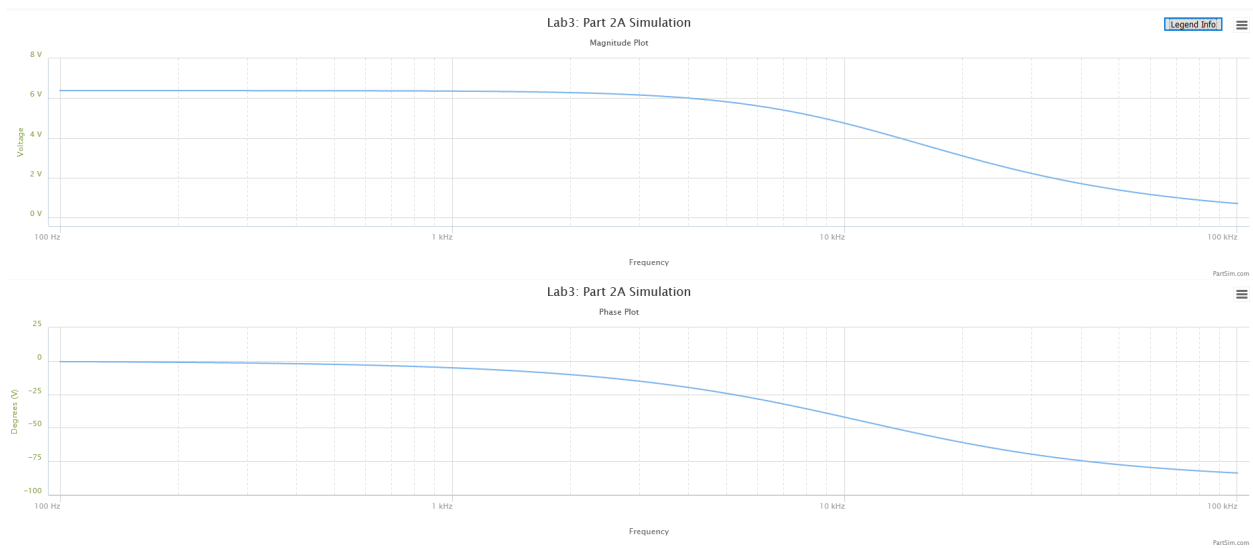


Figure 4: Bode plots for Part 2A

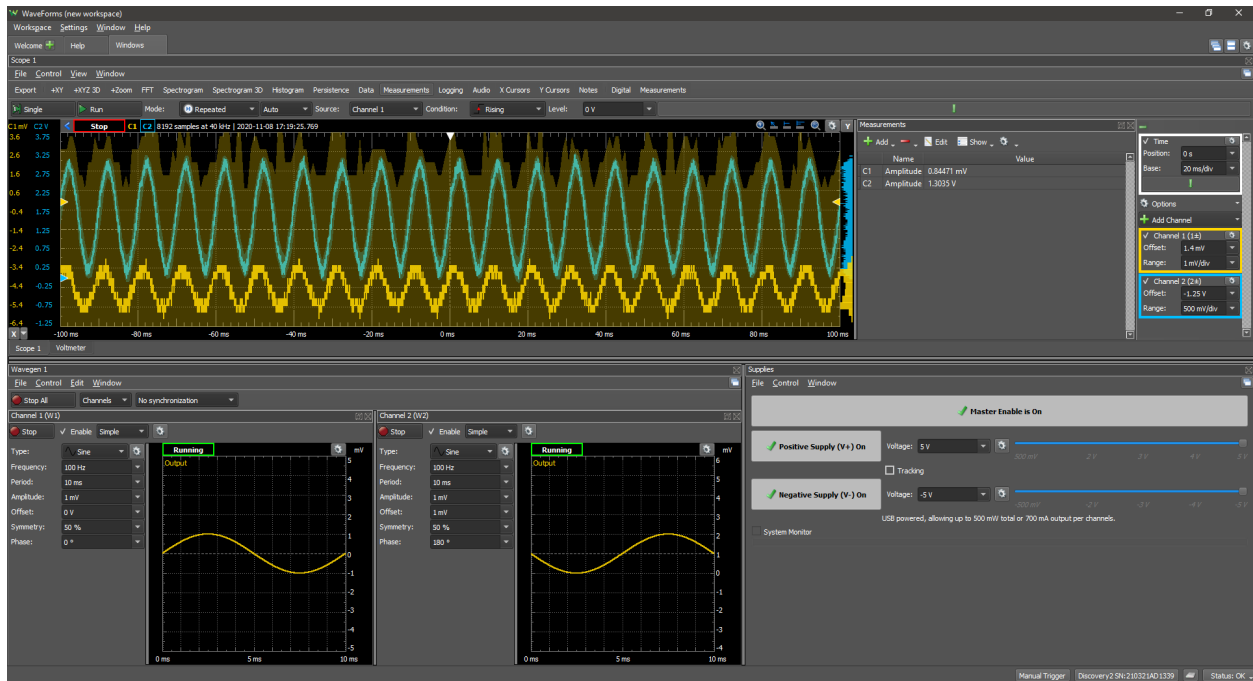


Figure 5: Waveforms Window for Part 2B

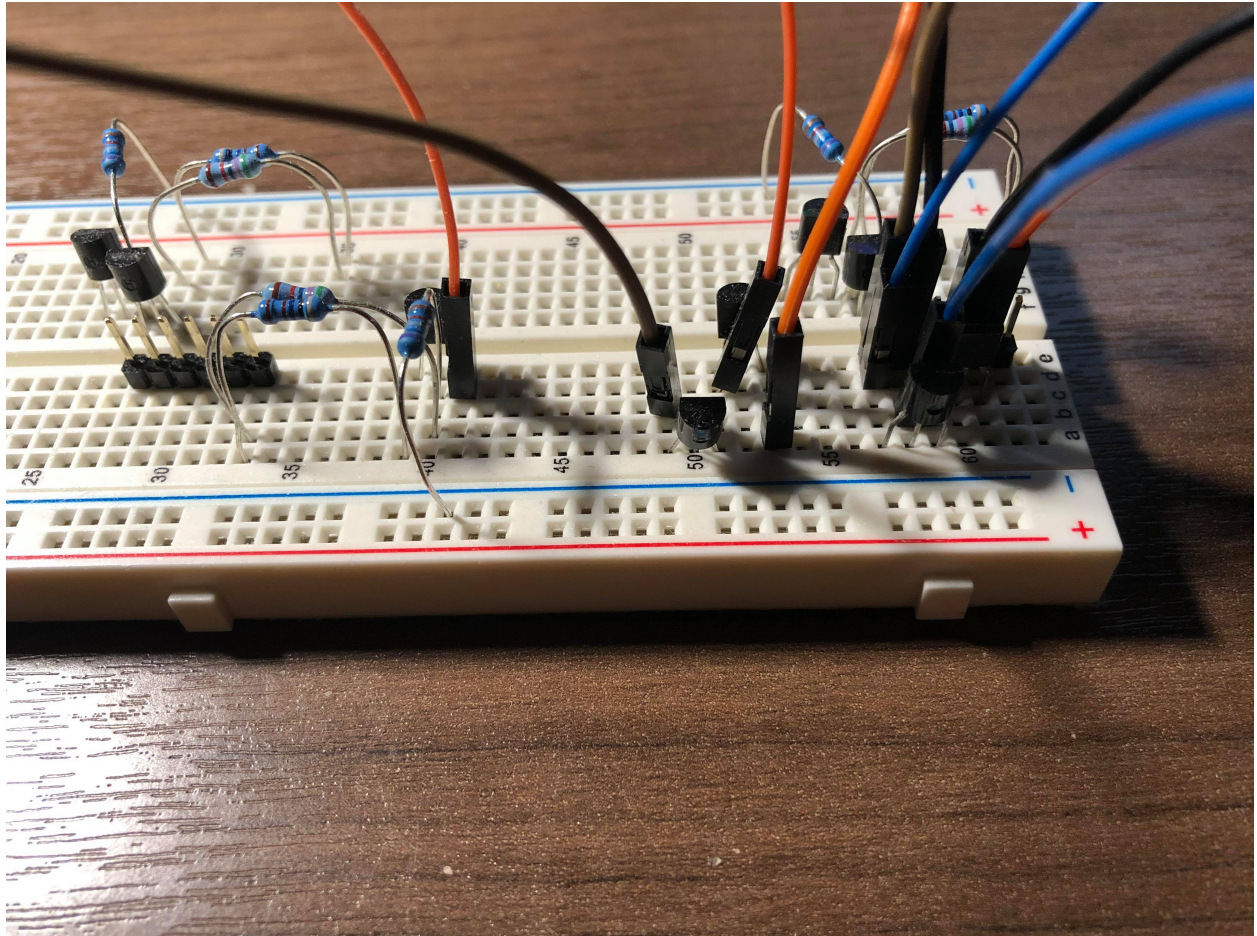


Figure 6: Circuit for Part 2B