

ELECENG 3EJ4 Lab 5

Raeed Hassan
hassam41
McMaster University

December 12, 2020

Part 1

Q1. 1. The transfer function can be derived:

$$\begin{aligned}
 T(s) &= \frac{V_o(s)}{V_{in}(s)} \\
 V_+ &= V_- \\
 V_- &= V_o(s) \frac{R_3}{R_2 + R_3} \\
 \frac{V_{in} - V_+}{R_1} &= V_+ s C_1 \\
 \frac{V_{in} - V_o \frac{R_3}{R_2 + R_3}}{R_1} &= V_o \frac{R_3}{R_2 + R_3} s C_1 \\
 \frac{V_o(s)}{V_{in}(s)} &= \frac{R_3 + R_2}{R_3(R_1 s C_1 + 1)} \\
 T(s) &= \frac{R_3 + R_2}{R_3(R_1 s C_1 + 1)}
 \end{aligned}$$

The transfer function is $T(s) = \frac{R_3 + R_2}{R_3(R_1 s C_1 + 1)}$, the low-frequency gain ($T(s)$ at $s = 0$) is 1.5 (approximately 3.52 dB), the -3dB frequency f_o is $f_o = \frac{1}{2\pi R_1 C_1} = 1591 \text{ Hz}$.

2. The simulated low frequency-gain and -3dB frequency f_o are 1.5 V/V (3.52 dB) and approximately 1.6 KHz. The measured low frequency-gain and -3dB frequency f_o are 3.53 dB and approximately 1.6 KHz. The simulated and measured values are in-line with the expected values from the calculations. The simulated and measured values are extremely close to each other. The transfer function for the simulated and measured data in Steps 1.3 and 1.8 is shown in Figure 3.

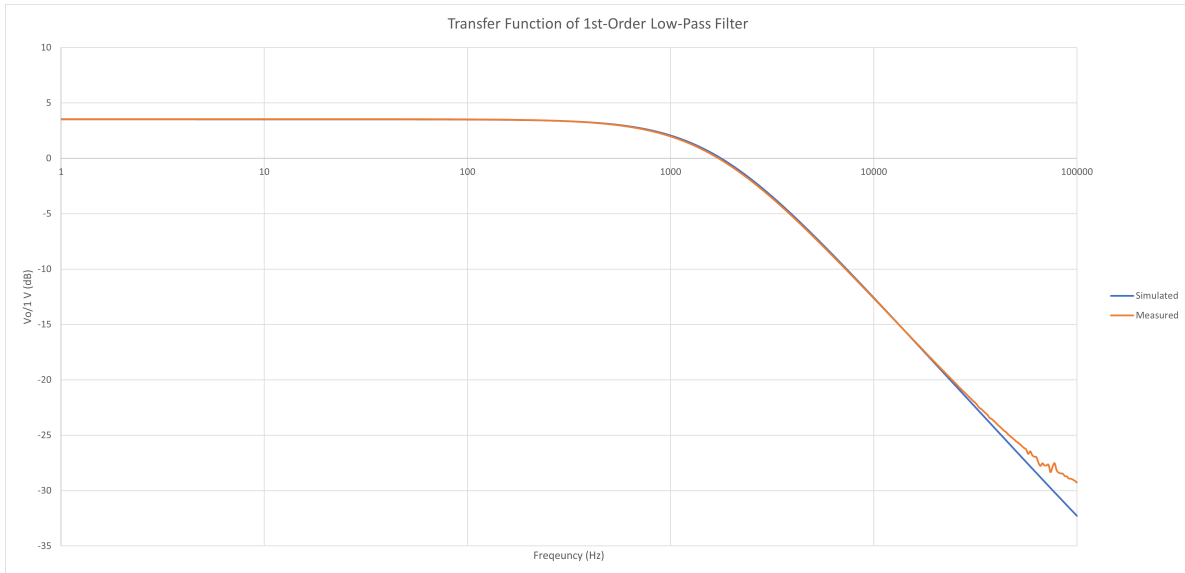


Figure 1: Transfer Function for 1st-Order Low-Pass Filter in Part 1

Part 2

Q2.

$$\begin{aligned}
 T(s) &= \frac{V_o(s)}{V_{in}(s)} \\
 0 &= \frac{V_1 - V_{in}}{R_1} + \frac{V_1 - V_o}{1/sC - 1} + \frac{V_1}{R_2 + 1/sC_2} \\
 V_2 &= V_3 \\
 V_2 &= V_1 \left(\frac{1/sC_2}{R_2 + 1/sC_2} \right) = V_3 = V_o \frac{R_3}{R_3 + R_4} \\
 \frac{V_o}{V_{in}} = T(s) &= \frac{R_3 + R_4}{s^2(C_1C_2R_1R_2R_3) + s(C_2R_2R_3 + C_2R_1R_3 - C_1R_1R_4) + R_3} \\
 &= \frac{200000}{s^2(0.0022) + s(34) + 100000} \\
 &= \frac{200000(1/0.0022)}{s^2 + s(\frac{34}{0.0022}) + 100000(1/0.0022)} \\
 &= \frac{1}{1.1 \times 10^{-8}s^2 + 1.7 \times 10^{-4}s + 0.5} \\
 Q &\approx 0.436
 \end{aligned}$$

The low-frequency gain (let $s = 0$) is equal to 2, which roughly matches the simulated low-frequency gain (6.02 dB or approximately 2 V/V) and the measured low-frequency gain (6.06 dB or approximately 2 V/V).

Q3. The pole frequencies can be found by factoring the transfer function $T(s)$, to get $s = -11503$ or $s = -3951$. Converting this to frequency, we get $f = 1830$ Hz or $f = 629$ Hz. The f_{max} is at the start (1 Hz), due to the transfer function having no zeros, and the peak value of the magnitude is the low-frequency gain.

	Calculated	Measured	Simulated
pole frequency f_o (Hz)	629	600	600
cut-off frequency f_c (Hz)	400	407	402
pole quality factor Q	0.436	N/A	N/A
peak value of the magnitude of the transfer function (dB)	6	6.02	6.06
frequency f_{max} (Hz)	1	1	1

Table 1: Question 3

The measured and simulated values generally matched the calculated values.

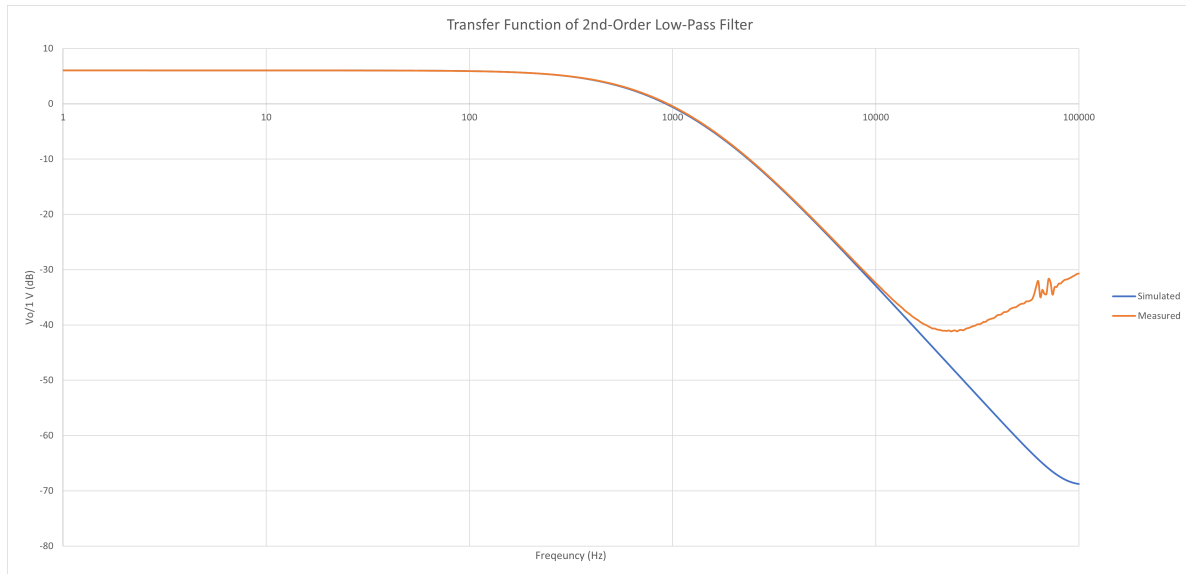


Figure 2: Transfer Function for 2nd-Order Low-Pass Filter in Part 2

Part 3

Q4.

$$0 = \frac{V_1 - V_{in}}{R_1} + \frac{V_1 - V_o}{1/sC_1} + \frac{V_1}{1/sC_2}$$

$$-\frac{V_1}{1/sC_2} = \frac{V_o}{R_2}$$

$$\frac{V_o}{V_{in}} = T(s) = \frac{1}{-1/R_2sC_2 - \frac{C_1R_1}{C_2R_2} - R_1/R_2 - R_1sC_1}$$

The simulated and measured center frequency gain were found by approximately -6 dB and -6.3 dB.

Q5. The center frequency can found by :

	Calculated	Measured	Simulated
center frequency (Hz)		600	600
pole quality factor		N/A	N/A
pole frequencies			
3-dB bandwidth (Hz)		1292	1342

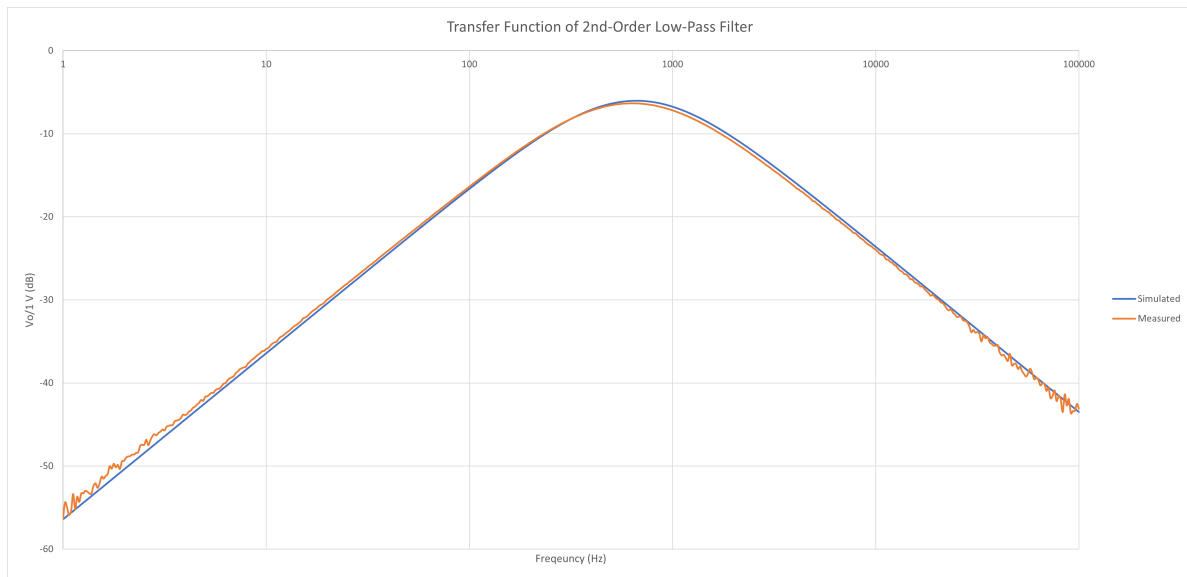


Figure 3: Transfer Function for 2nd-Order Band-Pass Filter in Part 3